

**NADAR SARASWATHI COLLEGE OF ENGINEERING AND TECHNOLOGY, THENI.**



<b>Course/Branch</b> : BE/EEE	<b>Year / Semester</b> :III/V	Format No.	NAC/TLP-07a.13
<b>Subject Code</b> :EE8553	<b>Subject Name</b> :Power Electronics	Rev. No.	02
<b>Unit No</b> :2	<b>Unit Name</b> :Phase controlled converters	Date	30.09.2020

**OBJECTIVE TYPE QUESTION BANK**

<b>S. No</b>	<b>Objective Questions (MCQ /True or False / Fill up with Choices )</b>	<b>BTL</b>
1	In a three-phase half-wave rectifier, each diode conducts for a duration of A) 120° B) 180° C) 90° D) 60°000	L2
2	A fully controlled natural commutated 3-phase bridge rectifier is operating with a firing angle $\alpha = 30^\circ$ . The peak to peak voltage ripple expressed as a ratio of the peak output dc voltage at the output of the converter bridge is A) $\sqrt{3}/2$ B) $2/\sqrt{3}$ C) 1 D) <b>0.5</b>	L3
3	A three-phase, three-pulse, M-3 type controlled converter uses _____ number of SCRs. A) 1 B) <b>3</b> C) 2 D) 4	L3
4	A three-phase, three-pulse, M-3 type controlled converter has firing angle for one of the SCRs set as $15^\circ$ . This SCR would start conducting at A) $0^\circ$ B) $15^\circ$ C) $30^\circ$ D) <b><math>45^\circ</math></b>	L3
5	In a three-phase, three-pulse, M-3 type controlled converter T1 starts to conduct at $30 + n^\circ$ . At what angles do T2 and T3 start to conduct? Assume that the conduction sequence is T1-T2-T3. A) $2n^\circ$ and $3n^\circ$ B) <b><math>150 + n^\circ</math> and <math>270 + n^\circ</math></b> C) $n^\circ$ each D) $30 + n^\circ$ and $60 + n^\circ$	L3
6	A three-phase three pulse type controlled converter is constructed using 3 SCR devices. The circuit is supplying an R load with $\alpha < 30^\circ$ . As such, each SCR device would conduct for A) $180^\circ$ each cycle B) <b><math>120^\circ</math> each cycle</b> C) $360^\circ$ each cycle D) $60^\circ$ each cycle	L2
7	In the circuit shown below, SCR T1 conducts first. If T1 is fired at an angle of $\alpha > 30^\circ$ , then T1 would conduct from	L3

Course/Branch : BE/EEE	Year / Semester :III/V	Format No.	NAC/TLP-07a.13
Subject Code :EE8553	Subject Name :Power Electronics	Rev. No.	02
Unit No :2	Unit Name :Phase controlled converters	Date	30.09.2020


**OBJECTIVE TYPE QUESTION BANK**

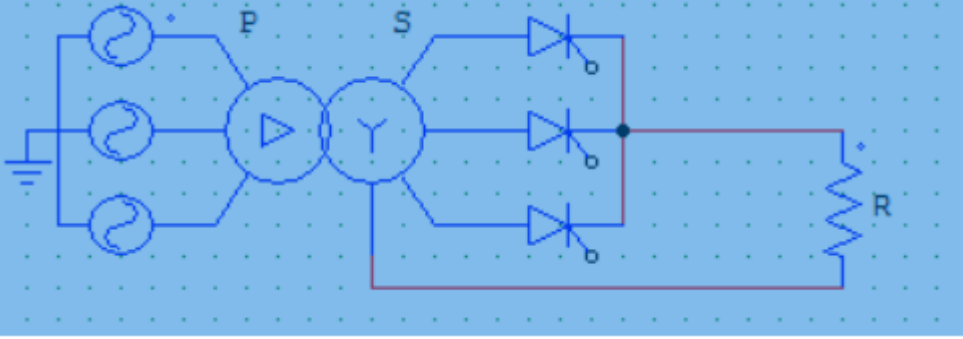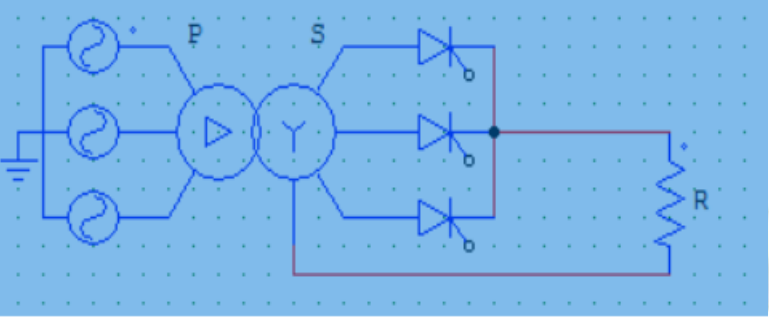	 <p>A) <math>\alpha</math> to <math>180^\circ</math>          B) <math>30 + \alpha</math> to <math>180^\circ</math>          C) <math>30 + \alpha</math> to <math>150^\circ</math>          D) <math>30 + \alpha</math> to <math>120^\circ</math></p>	
8	<p>Find the expression for average output voltage for the given circuit if firing angle is greater than <math>30^\circ</math>. Take <math>V_{mp}</math> = secondary side maximum value of phase voltage.</p>  <p>A) <math>(3\sqrt{3}V_{mp}/2\pi) \times \cos\alpha</math>  <b>B) <math>(3\sqrt{3}V_{mp}/2\pi) \times [1+\cos(30+\alpha)]</math>.</b>          C) <math>(3\sqrt{3}V_{mp}/2\pi) \times (1+\cos\alpha)</math>          D) <math>(3\sqrt{3}V_{mp}/2\pi) \times [3+\cos(30+\alpha)]</math>.</p>	L3
9	<p>In a 3-phase semi-converter, firing angle is less than <math>60^\circ</math>, as such each SCR and diode conduct respectively for _____ (in degrees)</p> <p>A) 60, 60  <b>B) 120, 120</b>          C) 90, 30          D) 180, 180</p>	L2
10	<p>A fully controlled converter uses</p> <p>A) both diodes and thyristors  <b>B) thyristors only</b>          C) diodes only          D) none of the mentioned</p>	L2
11	<p>A single phase full-converter using R load is a _____ quadrant converter and that using an RL load without FD is a _____ quadrant converter</p> <p>A) one, one  <b>B) one, two</b>          C) two, one</p>	L2

# NADAR SARASWATHI COLLEGE OF ENGINEERING AND TECHNOLOGY, THENI.

Course/Branch : BE/EEE	Year / Semester : III/V	Format No.	NAC/TLP-07a.13
Subject Code : EE8553	Subject Name : Power Electronics	Rev. No.	02
Unit No : 2	Unit Name : Phase controlled converters	Date	30.09.2020

## OBJECTIVE TYPE QUESTION BANK

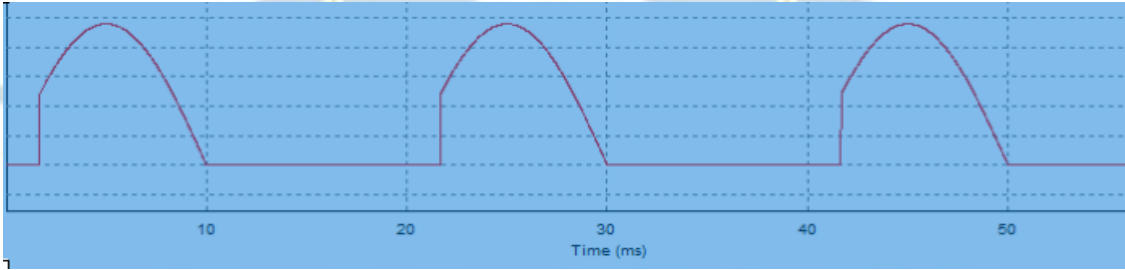	D) two, two	
12	A single phase full controlled bridge converter (B-2) uses A) 4 SCRs and 2 diodes B) 6 SCRs C) 4 SCRs and 4 diodes <b>D) 4 SCRs</b>	L2
13	In a Bridge type full controlled bridge converter <b>A) two SCRs conduct at a time</b> B) three SCRs conduct at a time C) four SCRs conduct at a time D) one SCRs conduct at a time	L2
14	The average output voltage is maximum when SCR is triggered at $\omega t =$ <b>A) 0</b> B) $\pi$ C) $\pi/2$ D) $\pi/4$	L2
15	For a certain SCR configuration, the below shown waveform is obtained. Find the value of the average output voltage with $\alpha = 30^\circ$ & $V_s = 240$ V.   <b>A) 100.8 V</b> B) 50.27 V C) 100 D) 120	L3
16	In the process of diode based rectification, alternating input voltage is converted into a) an uncontrolled alternating output voltage <b>b) an uncontrolled direct output voltage</b> c) a controlled alternating output voltage d) a controlled direct output voltage	L2
17	In a half-wave rectifier, the a) current & voltage both are bi-directional b) current & voltage both are uni-directional <b>c) current is always uni-directional but the voltage can be bi-directional or uni-directional</b> d) current can be bi-directional or uni-directional but the voltage is always uni-directional	L2

**NADAR SARASWATHI COLLEGE OF ENGINEERING AND TECHNOLOGY, THENI.**

<b>Course/Branch</b> : BE/EEE	<b>Year / Semester</b> :III/V	Format No.	NAC/TLP-07a.13
<b>Subject Code</b> :EE8553	<b>Subject Name</b> :Power Electronics	Rev. No.	02
<b>Unit No</b> :2	<b>Unit Name</b> :Phase controlled converters	Date	30.09.2020


**OBJECTIVE TYPE QUESTION BANK**

18	For a certain diode based rectifier, the output voltage (average value) is given by the equation $\frac{1}{2\pi} \int V_m \sin \omega t d(\omega t)$ Where the integral runs from 0 to $\pi$ The rectifier configuration must be that of a a) single phase full wave with R load b) single phase full wave with RL load <b>c) single phase half wave with R load</b> d) single phase half wave with RL load	L3
19	For a single phase half wave rectifier, with R load, the diode is reversed biased from $\omega t =$ a) 0 to $\pi$ , $2\pi$ to $2\pi/3$ <b>b) <math>\pi</math> to <math>2\pi</math>, <math>2\pi/3</math> to <math>3\pi</math></b> c) $\pi$ to $2\pi$ , $2\pi$ to $2\pi/3$ d) 0 to $\pi$ , $\pi$ to $2\pi$	L2
20	In a 1-Phase HW diode rectifier with R load, the average value of load current is given by Take Input (Vs) = $V_m \sin \omega t$ a) $V_m/R$ b) $V_m/2R$ <b>c) <math>V_m/\pi R</math></b> d) Zero	L2
21	In a semi-converter with RLE load during the freewheeling period, the energy is a) fed back to the source b) fed to the inductor(L) and absorbed by E c) absorbed by the L & E and dissipated at R <b>d) fed to the L &amp; E and dissipated at R</b>	L2
22	A single-phase symmetrical semi-converter employs <b>a) one SCR and one diode in each leg</b> b) two SCRs and two diodes in each leg c) two SCRs in each leg d) two diodes in each leg	L2
23	A single-phase asymmetrical semi-converter employs a) one SCR and one diode in each leg <b>b) two SCRs in one leg and two diodes in the other</b> c) two SCRs in both the legs d) two diodes in both the legs	L2
24	Dual converters provide a) two quadrant operation b) three quadrant operation <b>c) four quadrant operation</b> d) none of the mentioned	L2
25	A dual converters has a) two full converters in series b) two half converters in series <b>c) two full converters in anti-parallel</b>	L2

# NADAR SARASWATHI COLLEGE OF ENGINEERING AND TECHNOLOGY, THENI.

Course/Branch : BE/EEE	Year / Semester : III/V	Format No.	NAC/TLP-07a.13
Subject Code : EE8553	Subject Name : Power Electronics	Rev. No.	02
Unit No : 2	Unit Name : Phase controlled converters	Date	30.09.2020

## OBJECTIVE TYPE QUESTION BANK

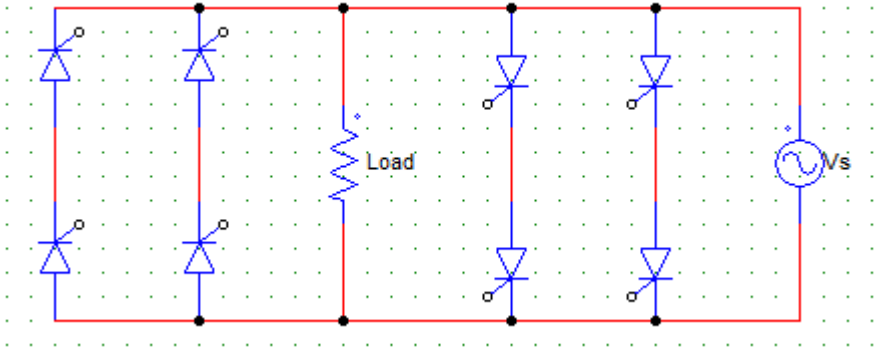	d) two half converters in anti-parallel	
26	<p>The major advantage of using dual converters is that</p> <p>a) it is cheaply available</p> <p>b) it has better pf</p> <p><b>c) no mechanical switch is required to change the mode of operation</b></p> <p>d) its operating frequency is very high</p>	L2
27	<p>Find the error in the below given dual converter circuit.</p>  <p>i) Load is not connected in the right position</p> <p>ii) Only 4 SCRs must be used</p> <p>iii) Voltage source is not connected for one of the converter circuit</p> <p>iv) Voltage source is not connected in the proper place</p> <p>a) All 4</p> <p>b) Both (i) and (iv)</p> <p><b>c) Both (iii) and (iv)</b></p> <p>d) Both (ii) and (iii)</p>	L3
28	<p>In case of controlled rectifiers, the nature of the load current (continuous or discontinuous) depends upon the</p> <p><b>a) type of load and firing angle</b></p> <p>b) only on the type of load</p> <p>c) only on the firing angle</p> <p>d) it is independent of all the parameters</p>	L2
29	<p>For a single phase half-wave thyristor circuit with R load, the power delivered to the resistive load is</p> <p>a) (average load voltage) x (average load current)</p> <p>b) (rms supply voltage)<sup>2</sup>/R</p> <p><b>c) (rms load voltage)<sup>2</sup>/R</b></p> <p>d) (average load voltage)/R</p>	L2
30	<p>For a single phase half-wave thyristor circuit with R load, the input power factor is given by</p> <p>a) rms source voltage/total rms line current</p> <p>b) rms input power/power delivered to the load</p> <p>c) cos <math>\alpha</math></p> <p><b>d) power delivered to load/input VA</b></p>	L2