 




NSCET E-LEARNING PRESENTATION

LISTEN ... LEARN... LEAD...






DEPARTMENT OF ELECTRICAL AND ELECTRONICS



II YEAR / IIIrd SEMESTER

EE8351– DIGITAL LOGIC CIRCUITS

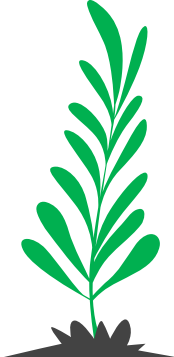

**M ARIVALAGAN M.Tech., (Ph. D), M.I.S.T.E.,
Assistant Professor & HOD /EEE
Nadar Saraswathi College of & Technology,
Vadapudupatti, Annanji (po), Theni – 625531.**



UNIT – V

VHDL

Introduction

- Hardware description languages (HDL)
 - Language to describe hardware
 - Two popular languages
 - **VHDL: Very High Speed Integrated Circuits Hardware Description Language**
 - Developed by DOD from 1983
 - IEEE Standard 1076-1987/1993/200x
 - Based on the ADA language
 - **Verilog**
 - IEEE Standard 1364-1995/2001/2005
 - Based on the C language

Applications of HDL

- Model and document digital systems
 - Different levels of abstraction
 - Behavioral, structural, etc.
- Verify design
- Synthesize circuits
 - Convert from higher abstraction levels to lower abstraction levels

Input-Output specification of circuit

- Example: my_ckt
 - Inputs: A, B, C
 - Outputs: X, Y
- VHDL description:



```
entity my_ckt is
port (
    A: in bit;
    B: in bit;
    S: in bit;
    X: out bit;
    Y: out bit);
end my_ckt ;
```

VHDL entity

```
entity my_ckt is  
port (  
  A: in bit;  
  B: in bit;  
  S: in bit;  
  X: out bit;  
  Y: out bit;  
);
```

Datatypes:

- In-built
- User-defined

▪ Filename same as circuit name
recommended

▪ Example:

- Circuit name: my_ckt
- Filename: my_ckt.vhd

Direction of port
3 main types:

Note the absence of semicolon ";" at the end of the last signal and the presence at the end of the closing bracket

Port names or
Signal names

ckt;

Built-in Datatypes

- Scalar (single valued) signal types:
 - `bit`
 - `boolean`
 - `integer`
 - Examples:
 - `A: in bit;`
 - `G: out boolean;`
 - `K: out integer range -2**4 to 2**4-1;`
- Aggregate (collection) signal types:
 - `bit_vector`: array of bits representing binary numbers
 - `signed`: array of bits representing signed binary numbers
 - Examples:
 - `D: in bit_vector(0 to 7);`
 - `E: in bit_vector(7 downto 0);`
 - `M: in signed(4 downto 0);`
`--signed 5 bit vector binary number`

User-defined datatype

- Construct datatypes arbitrarily or using built-in datatypes
- Examples:
 - `type temperature is (high, medium, low);`
 - `type byte is array(0 to 7) of bit;`

Functional specification

- Example:
 - Behavior for output X:
 - When $S = 0$
 $X \leq A$
 - When $S = 1$
 $X \leq B$
 - Behavior for output Y:
 - When $X = 0$ and $S = 0$
 $Y \leq '1'$
 - Else
 $Y \leq '0'$



VHDL Architecture

- VHDL description (sequential behavior):
`architecture arch_name of my_ckt is`
`begin`
`p1: process (A,B,S)`
`begin`
`if (S='0') then`
`X <= A;`
`else`
`X <= B;`
`end if;`

`if ((X = '0') and (S = '0')) then`
`Y <= '1';`
`else`
`Y <= '0';`
`end if;`

`end process p1;`
`end;`

Error: Signals defined as output ports can only be driven and not read

VHDL Architecture

```
architecture behav_seq of my_ckt is  
  signal Xtmp: bit;  
begin  
  p1: process (A, B, S, Xtmp)  
  begin  
    if (S='0') then  
      Xtmp <= A;  
    else  
      Xtmp <= B;  
    end if;  
  
    if ((Xtmp = '0') and (S = '0')) then  
      Y <= '1';  
    else  
      Y <= '0';  
    end if;  
  
    X <= Xtmp;  
  end process p1;  
end;
```

Signals can only be defined in this place before the **begin** keyword

General rule: Include all signals in the sensitivity list of the process which either appear in relational comparisons or on the right side of the assignment operator inside the **process construct.**

In our example:

Xtmp and **S** occur in relational comparisons
A, **B** and **Xtmp** occur on the right side of the assignment operators

VHDL Architecture

- VHDL description (concurrent behavior):

```
architecture behav_conc of my_ckt is
```

```
    signal Xtmp: bit;
```

```
begin
```

```
    Xtmp <= A when (S='0') else  
           B;
```

```
    Y <= '1' when ((Xtmp = '0') and (S = '0')) else  
         '0' ;
```

```
    X <= Xtmp;
```

```
end ;
```

Signals vs Variables

- Signals

- Signals follow the notion of 'event scheduling'
- An event is characterized by a (time,value) pair
- Signal assignment example:

X <= **Xtmp**; means

Schedule the assignment of the value of signal **Xtmp** to signal **X** at (Current time + delta)

where delta: infinitesimal time unit used by simulator for processing the signals

Signals vs Variables

- Variables
 - Variables do not have notion of 'events'
 - Variables can be defined and used only inside the **process** block and some other special blocks.
 - Variable declaration and assignment example:

```
process (...)  
variable K : bit;  
begin  
    ...  
    -- Assign the value of signal L to K  
    K := L;  
    ...  
end process;
```

Variables can only be defined and used inside the **process** construct and can be defined only in this place

ately

Simulation

- Simulation is modeling the output response of a circuit to given input stimuli
- For our example circuit:
 - Given the values of A, B and S
 - Determine the values of X and Y
- Many types of simulators used
 - Event driven simulator is used popularly
 - Simulation tool we shall use: ModelSim



Simulation

```
architecture behav_seq of my_ckt is
  signal Xtmp: bit;
```

```
begin
  p1: process (A,B,S,Xtmp)
    variable XtmpVar: bit;
  begin
```

```
    if (S='0') then
      Xtmp <= A;
    else
      Xtmp <= B;
    end if;
```

```
    if ((Xtmp = '0') and (S = '0')) then
      Y <= '1';
    else
      Y <= '0';
    end if;
```

```
    X <= Xtmp;
    XtmpVar := Xtmp;
  end process p1;
```

```
end;
```



Time 'T'	A	B	S	Xtmp	Y	XtmpVar	X
0-	1	1	1	'X'	'X'	'X'	'X'
0	0	1	0	'X'	'X'	'X'	'X'
0+d	0	1	0	0	0	0	'X'
0+2d	0	1	0	0	1	0	0
1	0	1	1	0	1	0	0
1+d	0	1	1	1	0	0	0
		1	1	1	0	0	1

Scheduled events

Scheduled events

executed:

Xtmp = 0

Y = 1

Scheduled events

list:

(empty)

d:

Synthesis

- Synthesis:
Conversion of behavioral level description to structural level netlist
 - Abstract behavioral description maps to concrete logic-level implementation
 - For ex. Integers at behavioral level mapped to bits at structural level
- Structural level netlist
 - Implementation of behavioral description
 - Describes interconnection of gates
- CAD tools are used to perform synthesis

Structural level netlist

- Behavior of our example circuit:
 - Behavior for output X:
 - When $S = 0$
 $X \leq A$
 - When $S = 1$
 $X \leq B$
 - Behavior for output Y:
 - When $X = 0$ and $S = 0$
 $Y \leq 1$
 - Else
 $Y \leq 0$



- Logic functions
 - $Sbar = \sim S$
 - $Xbar = \sim X$
 - $X = A*(Sbar) + B*S$
 - $Y = (Xbar)*(Sbar)$

Structural level netlist

```
architecture behav_conc of my_ckt is
  -- component declarations

  signal Sbar, Xbar, W1, W2: bit;

begin

  G1: not port map(Sbar, S);
  G2: and port map(W1, A, Sbar);
  G3: and port map(W2, B, S);
  G4: or port map(X, W1, W2);

  G5: not port map(Xbar, X);
  G6: and port map(Y, Xbar, Sbar);

end ;
```

- Gate level VHDL descriptions (**and**, **or**, etc) are described separately
- Design in which other design descriptions are included is called a “hierarchical design”
- A VHDL design is included in current design using port map statement

STRUCTURAL MODELING

1. Consider an example of a Dual 2 by 1 multiplexer using structural modeling.
2. Components required : 2- input AND gate
2- input OR gate Inverter

ENTITY inv IS

PORT(

i1: IN BIT;

o1: OUT BIT);

END inv;

```
ARCHITECTURE single_delay OF inv IS BEGIN
```

```
    o1 <= not (i1) after 5ns; END single_dela
```

```
y;
```

```
ARCHITECTURE single_delay OF inv IS BEGIN
```

```
    o1 <= not (i1) after 5ns; END
```

```
single_delay;
```

DESIGN OF A SIMPLE 2 INPUT AND GATE WITH A DELAY

ENTITY and2 IS

PORT(

i1, i2 :IN BIT; o1:

OUT BIT

);

END and2;

ARCHITECTURE single_delay OF and2 IS BEGIN

END o1 <= (i1 AND i2) after 8ns

single_delay;

DESIGN OF A SIMPLE 2 INPUT OR GATE WITH A DELAY

```
ENTITY or2 IS
    PORT(
        i1, i2 :IN BIT;
        o1:  OUT
        BIT);

END or2;
ARCHITECTURE single_delay OF
or2 IS BEGIN

ENDo1 <= (i1 or i2) after 8ns;
single_delay;
```


SINGLE AND DUAL 2-1 MULTIPLEXER ENTITY

ENTITY

single_mux IS

PORT(

 s: IN BIT ; --select input

 iA, iB : IN BIT; -- iA is selected

 if

 - s='0' and iB is selected if s='1'

EN single_mux OUT BIT --output of the mux

D x;);



THANKS!

Department of EEE, NSCET, Theni